

# Project Report: Design Your Own MIPS CPU and OS

## 1. Introduction

One of the course objectives is to design a complete CPU system. This starts with studying ISA, assembly language, ALU, datapath and control, and pipelining in theory. To make this learning effective, a step-by-step design of a complete CPU system was carried out using pen-and-paper, simulation tools, and simulated hardware.

The project involves designing a 32-bit single-cycle CPU with separate instruction and data memory, supported by an assembler, and tested using operating system-like programs. The CPU datapath and control unit were implemented in Verilog, and benchmark programs were used to validate execution.

## 2. ISA Study (Document + Program)

### 2.1 Overview of ISA Design

A 32-bit single-cycle CPU was designed with general-purpose instructions supporting arithmetic, logic, memory access, and control flow. Instruction formats include:

- **R-type:** Register operations (ADD, SUB, AND, OR, XOR, SLL, SRL) – implemented in `alu32.v` and `regfile32.v`.
- **I-type:** Immediate and memory operations (LW, SW, ADDI) – connected via `ram.v`, verified with `dmem.txt`.
- **J-type:** Control instructions (J, JAL, JR) – implemented in `control.v` and `datapath.v`.

The CPU has 8 general-purpose registers (R0–R7). R0 is fixed at 0; the others are used for arithmetic, logic, memory, and subroutine operations. Input/output operations are handled using `dmem.txt`, where LW and SW instructions simulate reading and writing data.

### 2.2 Input/Output Operations

Since external displays and keyboards cannot be connected, I/O is simulated via `dmem.txt`. Load (LW) and store (SW) instructions are used to read and write values, which represent program input and output. Results can be verified from the register file (`regfile32.v`) and memory content.

### 2.3 Design Requirements

- **Operands:** Register-based with memory access.

- **Instruction Set:** Arithmetic (ADD, SUB), Logical (AND, OR, XOR), Memory (LW, SW), Control (J, JAL, JR).
- **Registers:** 8 general-purpose (R0–R7).
- **Memory:** Data memory simulated in `dmem.txt`; instruction memory in `rom.v`, `memfile.txt`.
- **Files Used:** `alu32.v`, `regfile32.v`, `ram.v`, `control.v`, `datapath.v`, `insttest2.s`.

## 2.4 Benchmark Programs

Three types of programs were implemented:

1. **Arithmetic & Logic** – basic operations to test ALU.
2. **Conditional Checking** – branch instructions (BEQ) to validate decision making.
3. **Loop Programs & Subroutines** – `insttest2.s` modified to test JAL/JR and MIN, MAX, MEAN calculations.

## 2.5 Evaluation and Discussion

Benchmark programs executed correctly for arithmetic and logic operations. Subroutine calls using JAL/JR worked after modifying `datapath.v` and `control.v` to handle link registers and program counter updates. The AVG output remained 0, also sometimes 1 or 10 due to assembler branching issues, later identified and reported to faculty.

## 3. Assembler (Software)

The assembler translates `.s` assembly programs into machine code for instruction memory.

- **Language Used:** C++ (`finalassembler.cpp`)
- **Input Format:** Assembly text file (`.s`)
- **Output Format:** Binary (`no_address.bin`, `no_address.data`)

### 3.1 Design & Implementation

The assembler parses assembly instructions, converts them into machine code, and generates output files (`no_address.bin`, `no_address.data.bin`) compatible with Verilog RAM blocks.

**Files Used:** `insttest2.s`, `finalassembler.cpp`, `outp3.no_address.text.bin`, `outp3.no_address.data.bin`

### 3.2 Testing & Validation

Tested using `insttest2.s` to verify correct translation of JAL/JR and arithmetic instructions. Outputs were loaded into instruction memory (`rom.v`) for simulation in `MIPS_SCP.v`.

## 4. Operating System Based on MIPS Assembly

### 4.1 Program Design

- **Main Function:** Calls three subroutines (MAX, MIN, MEAN) using JAL/JR.
- **Subroutines:** Implemented using LI and SW instructions; divide subroutine provided for MEAN.
- **Input Data:** Ten integers loaded into registers and stored in `dmem.txt`.

### 4.2 Testing & Validation

- **Files Used:** `instttest2.s`
- **Execution:** Verified subroutine results in register file and `memfile.txt`, `dmem.txt`.
- **Observations:** MIN and MAX values computed correctly; MEAN remained 0, sometimes 1 or 10 due to assembler issue.

## 5. Full CPU (Verilog)

### 5.1 Datapath & Control Path Design

- **Components:** `alu32.v`, `regfile32.v`, `ram.v`, `control.v`, `datapath.v`
- **Connectivity:** Corrected for JAL/JR instructions and proper memory read/write.
- **Top-Level:** `MIPS_SCP.v` with testbench `MIPS_SCP_tb.v`.

### 5.2 Implementation Steps

- Write assembly code in `instttest2.s` with subroutine calls.
- Compile assembler (`finalassembler.cpp`) → generate `no_address.bin`, `outp3.no_address.text.bin`.
- Load binary into instruction memory (`rom.v`).
- Simulate in ModelSim (`MIPS_SCP_tb.v`) and verify execution.
- Check register file (`regfile32.v`) and data memory (`dmem.txt`) for results.


### 5.3 Challenges & Solutions



- **WSL/Windows Issues:** Resolved environment errors to run scripts.
- **ModelSim Installation Issues:** Reinstalled and configured correctly.
- **Compilation Issues:** Fixed signal connections in `datapath.v` and `ram.v`.
- **Benchmark Output Errors:** MIN/MAX correct; AVG 0/1/10 → traced to assembler branching.

- **Debugging Steps:** Verified machine code, updated control path for JAL/JR, re-tested subroutine execution.


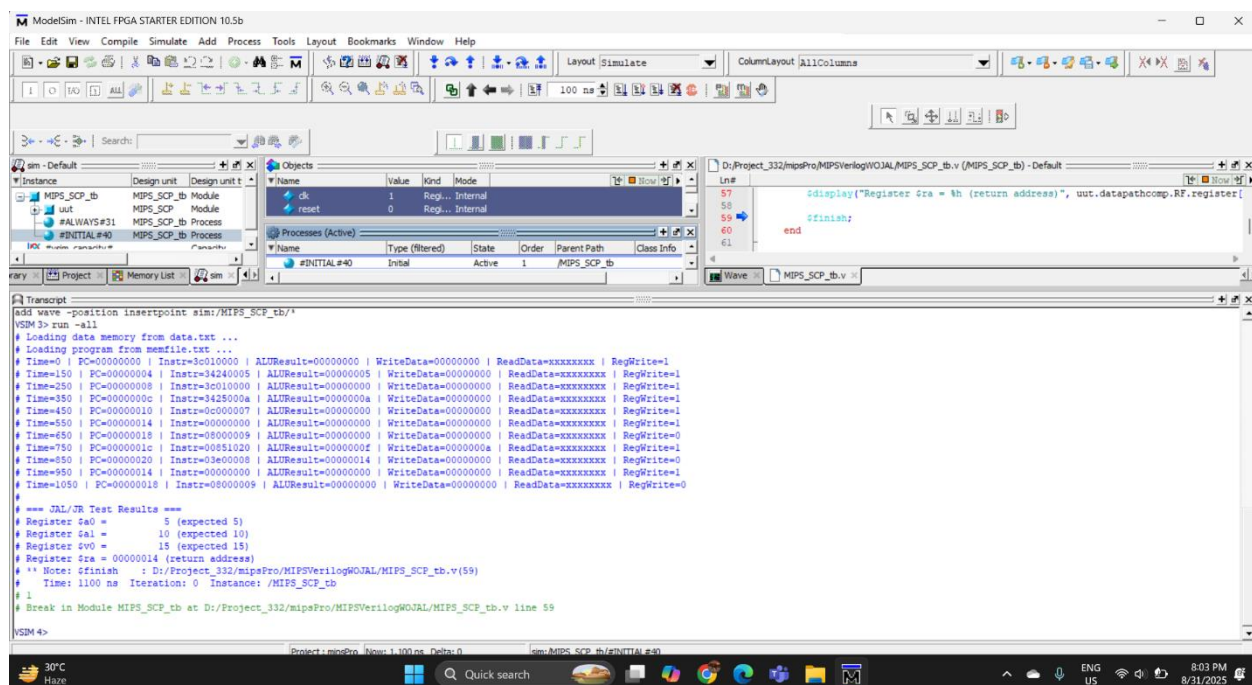
## 5.4 Testing & Validation

- **Verification:** Register file shows correct return addresses; data memory shows MIN and MAX outputs.
- **Simulation Outputs:** mips\_scp.vcd (For min max mean) and mips\_scp.vcd (jal jr test) verified instruction execution.
- **Screenshots:** Include data memory and register file content.
- **Files Submitted:** Verilog codes, assembly programs, simulation results, zipped folder.





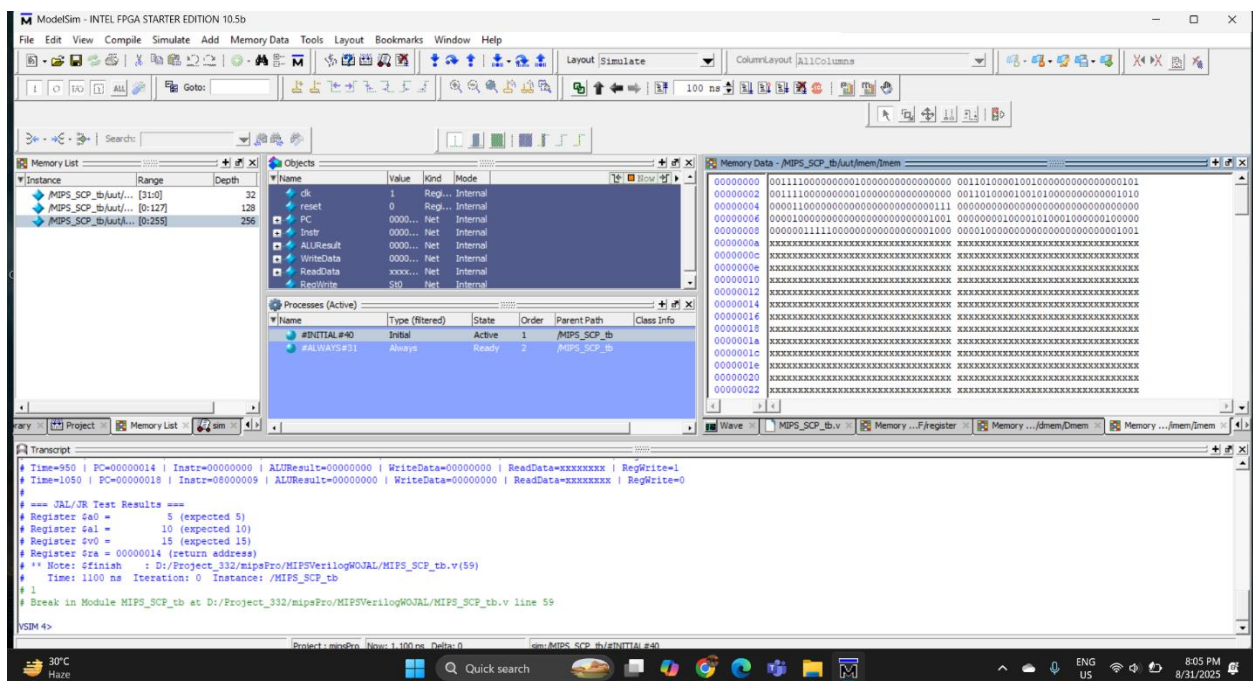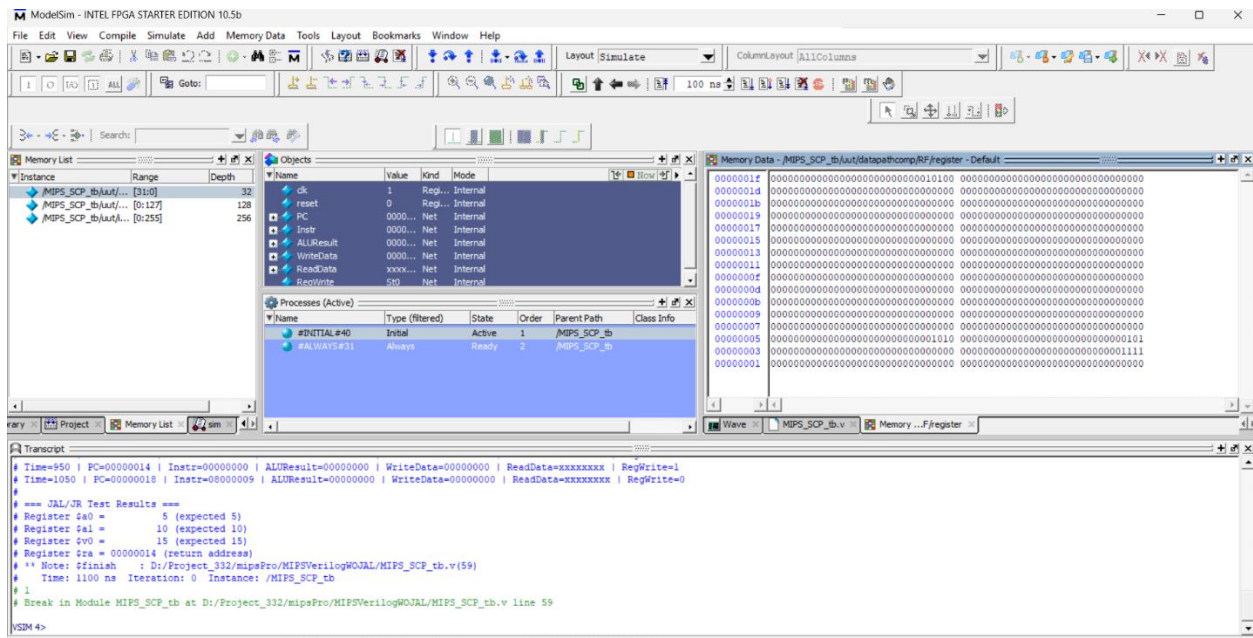

*Jal Jr Work Testing With memory list*

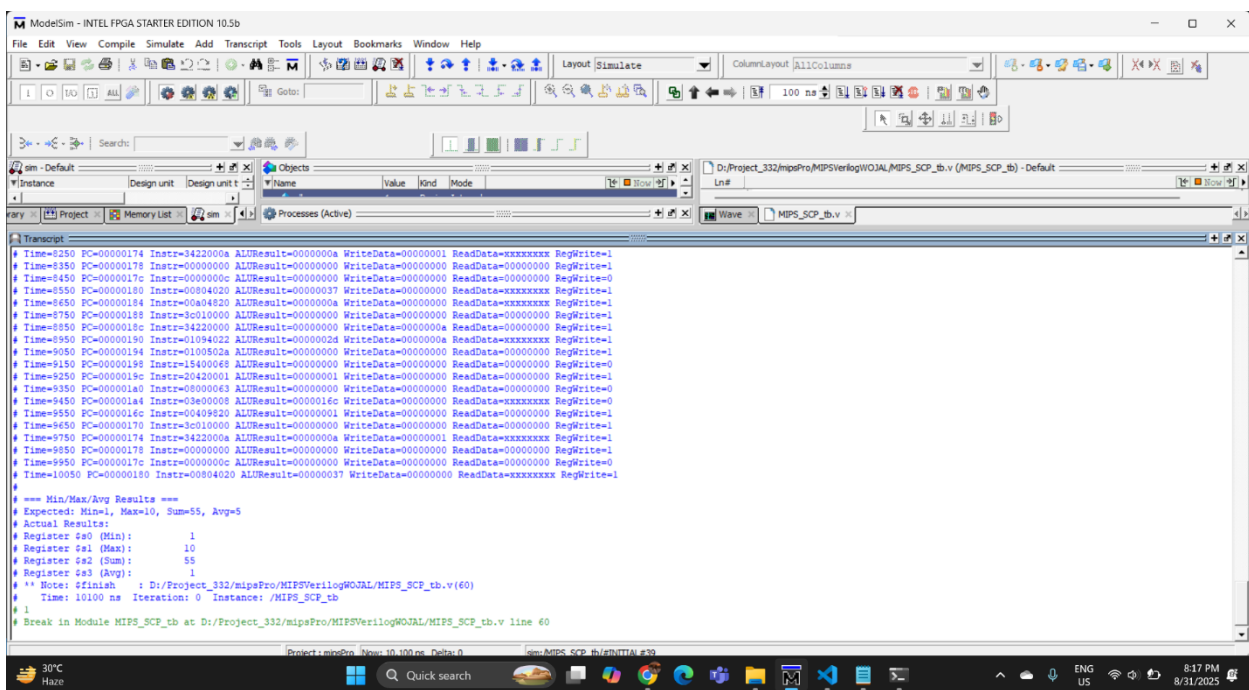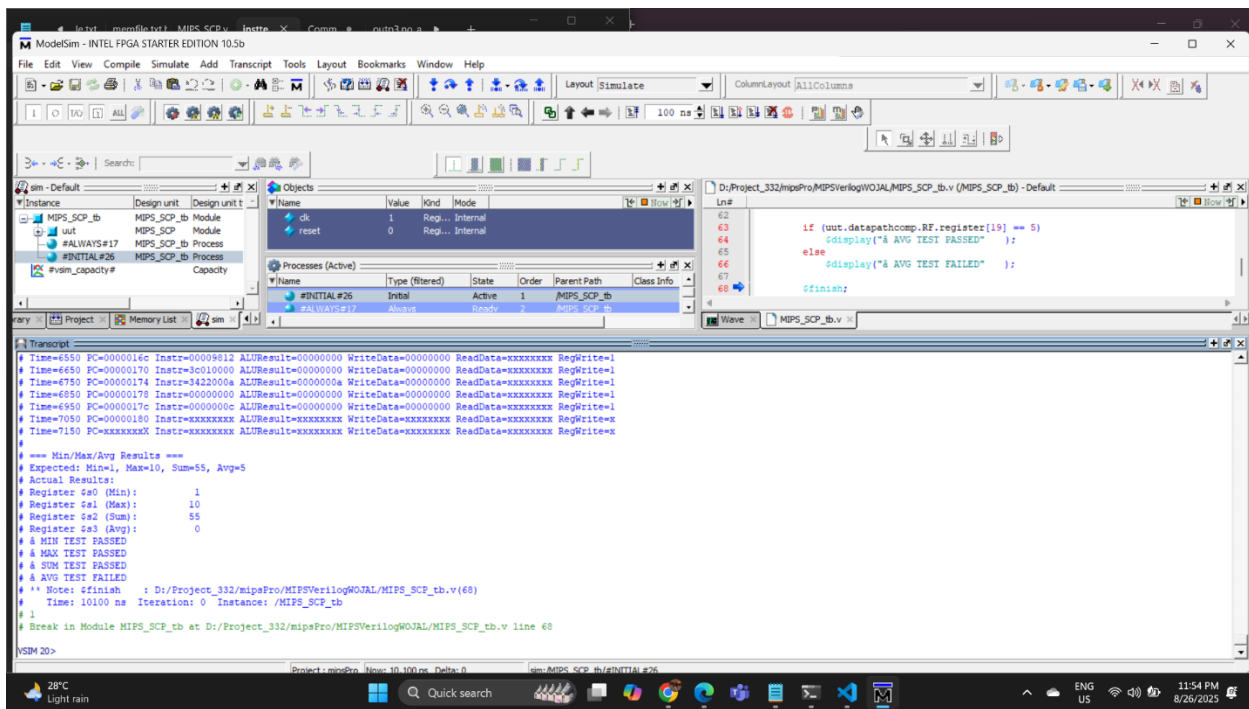



 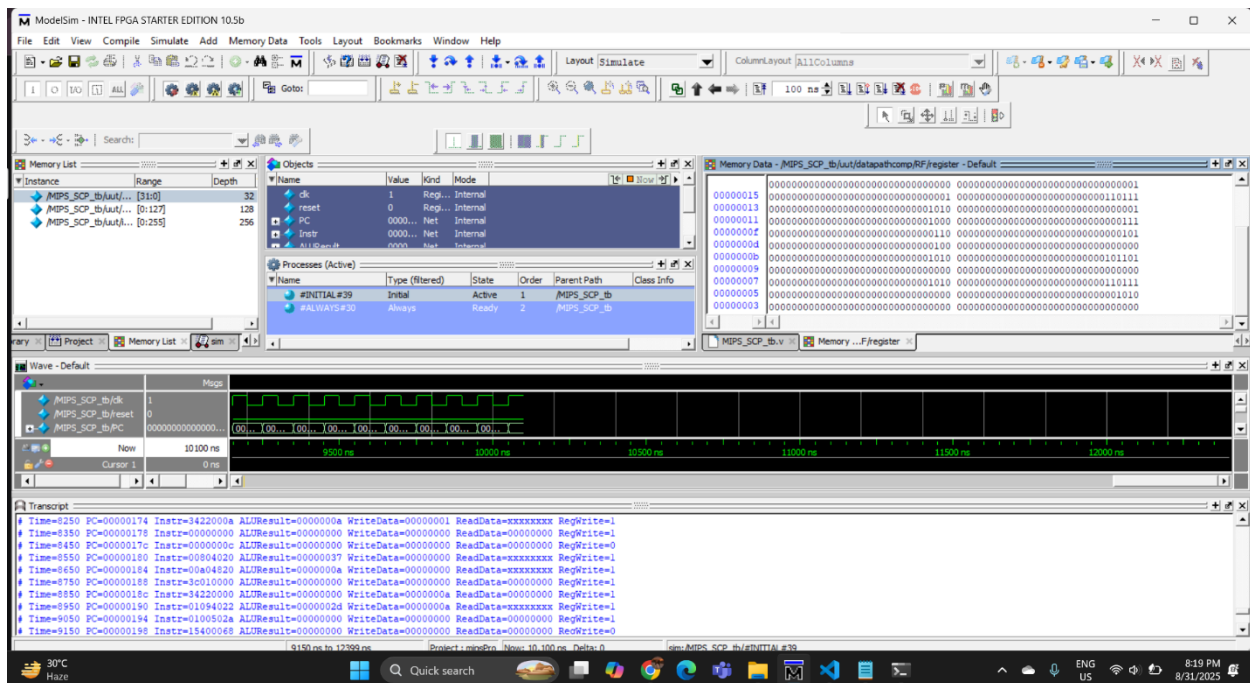

*MIN, MAX, and MEAN were tested with memory listings, showing varying average values due to assembler issues.*

## 6. Conclusion

The project successfully designed a 32-bit single-cycle CPU, developed an assembler, implemented subroutine programs (MIN, MAX, MEAN), and simulated the full CPU in Verilog. During the project, We faced and resolved challenges related to environment setup, assembler output, and datapath connectivity through systematic debugging. Through this process, We gained hands-on experience in ISA design, assembly programming, Verilog-based CPU implementation, and debugging complex hardware-software interactions. We would like to sincerely thank [Dr. Mohammad Abdul Qayum](#) for his guidance, support, and valuable teaching throughout the course, which greatly helped us complete this project.

## 7. References

- UpgradedMIPS32Assembler GitHub Repository :  
<https://github.com/RoySRC/UpgradedMIPS32Assembler.git>
- ModelSim Simulator
- ChatGPT and DeepSeek – used for debugging and assisting in code analysis.
- CSE332 Course Materials, North South University



## Codes

### //ram.v

```
`timescale 1ns/1ns
```

```
module ram(  
    input clk,  
    input we,  
    input [31:0] adr,  
    input [31:0] din,  
    output [31:0] dout  
);
```

```
    parameter depth = 128;  
    parameter width = 32;
```

```
    reg [width-1:0] Dmem [0:depth-1];
```

```
    // word addressing (ignore adr[1:0])  
    assign dout = Dmem[adr[31:2]];
```

```
    initial begin  
        $display("Loading data memory from  
data.txt ...");  
        $readmemb("dmem.txt", Dmem);  
    end
```

```
    always @(posedge clk) begin  
        if (we)  
            Dmem[adr[31:2]] <= din;  
    end
```

```
endmodule
```

### //rom.v

```
`timescale 1ns/1ns
```

```
module rom(  
    input [31:0] adr,  
    output [31:0] dout  
);
```

```
    parameter depth = 256;
```

```
    parameter width = 32;  
    reg [width-1:0] lmem [0:depth-1];
```

```
    initial begin  
        $display("Loading program from memfile.txt  
...");  
        $readmemb("memfile.txt", lmem);    //  
        binary instructions  
    end
```

```
    // Word addressing (ignore lower 2 bits)  
    assign dout = lmem[adr[31:2]];
```

```
endmodule
```

### // file: Datapath.v

```
`include "adder.v"  
`include "alu32.v"  
`include "flopr_param.v"  
`include "mux2.v"  
`include "mux4.v"  
`include "regfile32.v"  
`include "signext.v"  
`include "sl2.v"
```

```
`timescale 1ns/1ns
```

```
module Datapath(input clk,  
    input reset,  
    input RegDst,  
    input RegWrite,  
    input ALUSrc,  
    input Jump,  
    input Jal,  
    input Jr,  
    input MemtoReg,  
    input PCSrc,  
    input [3:0] ALUControl,  
    input [31:0] ReadData,  
    input [31:0] Instr,  
    output [31:0] PC,  
    output ZeroFlag,
```

```

        output [31:0] datatwo,
        output [31:0] ALUResult);

wire [31:0] PCNext, PCplus4, PCbeforeBranch,
PCBranch;
wire [31:0] extendedimm, extendedimmafter,
MUXresult, dataone, aluop2;
wire [4:0] writereg;
wire [31:0] PCNextFinal;

// PC Logic
flopr_param  #(32)  PCregister(clk,  reset,
PCNextFinal, PC);
adder #(32) pcadd4(PC, 32'd4, PCplus4);
slt2          shifteradd2(extendedimm,
extendedimmafter);
adder  #(32)  pcaddsigned(extendedimmafter,
PCplus4, PCbeforeBranch);
mux2      #(32)      branchmux(PCplus4,
PCbeforeBranch, PCSrc, PCBranch);
mux2      #(32)      jumpmux(PCBranch,
{PCplus4[31:28], Instr[25:0], 2'b00}, Jump,
PCNext);

// JR MUX - Select between normal next PC and
register value for JR
mux2  #(32)  jrmux(PCNext,  dataone,  Jr,
PCNextFinal);

// Register File
// Register File
registerfile32 RF(
    .clk(clk),
    .we(RegWrite),
    .reset(reset),
    .ra1(Instr[25:21]),
    .ra2(Instr[20:16]),
    .wa(writereg),
    .wd(MUXresult),
    .rd1(dataone),
    .rd2(datatwo)
);

```

```

// Write register selection MUX
mux4 #(5) write_reg_mux(
    .d0(Instr[20:16]), // rt (I-type)
    .d1(Instr[15:11]), // rd (R-type)
    .d2(5'b11111),    // $ra (for JAL)
    .d3(5'b00000),    // unused
    .s({Jal, RegDst}),
    .y(writereg)
);

// Write data selection MUX
mux4 #(32) result_mux(
    .d0(ALUResult), // ALU result
    .d1(ReadData),  // Memory read data
    .d2(PCplus4),   // Return address (for JAL)
    .d3(32'h00000000), // unused
    .s({Jal, MemtoReg}),
    .y(MUXresult)
);

// ALU
alu32 alucomp(
    .a(dataone),
    .b(aluop2),
    .f(ALUControl), // match "f"
    .shamt(Instr[10:6]),
    .y(ALUResult),  // match "y"
    .zero(ZeroFlag)
);

signext          immextention(Instr[15:0],
extendedimm);
mux2  #(32)  aluop2sel(datatwo, extendedimm,
ALUSrc, aluop2);

endmodule

```

# // Control Unit with JAL and JR support

```
`timescale 1ns/1ns
```

```
module ControlUnit(
    input [5:0] Opcode,
    input [5:0] Func,
    input Zero,
    output reg MemtoReg,
    output reg MemWrite,
    output reg ALUSrc,
    output reg RegDst,
    output reg RegWrite,
    output reg Jump,
    output reg Jal,
    output reg Jr,
    output PCSrc,
    output reg [3:0] ALUControl
);

reg [9:0] temp;
reg Branch, BNE;

always @(*) begin
    // Default values
    temp = 10'b0;
    ALUControl = 4'b0;
    Jal = 1'b0;
    Jr = 1'b0;
    Branch = 1'b0;
    BNE = 1'b0;

    case (Opcode)
        6'b000000: begin // R-type
            case (Func)
                6'b100000: begin // ADD
                    temp = 10'b1100000000;
                    ALUControl = 4'b0000;
                end
                6'b100001: begin // ADDU
                    temp = 10'b1100000000;
                    ALUControl = 4'b0000;
                end
            end
        end
    end
```

```
        6'b100010: begin // SUB
            temp = 10'b1100000000;
            ALUControl = 4'b0001;
        end
        6'b100011: begin // SUBU
            temp = 10'b1100000000;
            ALUControl = 4'b0001;
        end
        6'b100100: begin // AND
            temp = 10'b1100000000;
            ALUControl = 4'b0010;
        end
        6'b100101: begin // OR
            temp = 10'b1100000000;
            ALUControl = 4'b0011;
        end
        6'b100110: begin // XOR
            temp = 10'b1100000000;
            ALUControl = 4'b0100;
        end
        6'b100111: begin // NOR
            temp = 10'b1100000000;
            ALUControl = 4'b1010;
        end
        6'b101010: begin // SLT
            temp = 10'b1100000000;
            ALUControl = 4'b1000;
        end
        6'b101011: begin // SLTU
            temp = 10'b1100000000;
            ALUControl = 4'b1001;
        end
        6'b000000: begin // SLL
            temp = 10'b1100000000;
            ALUControl = 4'b0101;
        end
        6'b000010: begin // SRL
            temp = 10'b1100000000;
            ALUControl = 4'b0110;
        end
        6'b000011: begin // SRA
            temp = 10'b1100000000;
```

```

        ALUControl = 4'b0111;
    end
    6'b000100: begin          // SLLV
        temp = 10'b1100000000;
        ALUControl = 4'b1011;
    end
    6'b000110: begin          // SRLV
        temp = 10'b1100000000;
        ALUControl = 4'b1100;
    end
    6'b000111: begin          // SRAV
        temp = 10'b1100000000;
        ALUControl = 4'b1101;
    end
    6'b001000: begin          // JR
        temp = 10'b0000000001;
        ALUControl = 4'b0000;
        Jr = 1'b1;
    end
    default: begin
        temp = 10'b0000000000;
        ALUControl = 4'b0000;
    end
endcase
end

6'b100011: begin            // LW
    temp = 10'b1010010000;
    ALUControl = 4'b0000;
end

6'b101011: begin            // SW
    temp = 10'b0010100000;
    ALUControl = 4'b0000;
end

6'b000100: begin            // BEQ
    temp = 10'b0001000000;
    ALUControl = 4'b0001;
    Branch = 1'b1;
end

```

```

6'b000101: begin            // BNE
    temp = 10'b0001000000;
    ALUControl = 4'b0001;
    Branch = 1'b1;
    BNE = 1'b1;
end

6'b001000: begin            // ADDI
    temp = 10'b1010000000;
    ALUControl = 4'b0000;
end

6'b001001: begin            // ADDIU
    temp = 10'b1010000000;
    ALUControl = 4'b0000;
end

6'b001100: begin            // ANDI
    temp = 10'b1010000000;
    ALUControl = 4'b0010;
end

6'b001101: begin            // ORI
    temp = 10'b1010000000;
    ALUControl = 4'b0011;
end

6'b001110: begin            // XORI
    temp = 10'b1010000000;
    ALUControl = 4'b0100;
end

6'b001010: begin            // SLTI
    temp = 10'b1010000000;
    ALUControl = 4'b1000;
end

6'b001011: begin            // SLTIU
    temp = 10'b1010000000;
    ALUControl = 4'b1001;
end

```

```

        6'b000010: begin                // J
            temp = 10'b0000001000;
            ALUControl = 4'b0000;
            Jump = 1'b1;
        end

        6'b000011: begin                // JAL
            temp = 10'b1000001000;
            ALUControl = 4'b0000;
            Jump = 1'b1;
            Jal = 1'b1;
        end

        6'b001111: begin                // LUI
            temp = 10'b1010000000;
            ALUControl = 4'b1110;
        end

        default: begin                  // NOP
            temp = 10'b0000000000;
            ALUControl = 4'b0000;
        end
    endcase

    // Use blocking assignment for the
    concatenation
    {RegWrite, RegDst, ALUSrc, MemWrite,
    MemtoReg, Jump} = temp[9:4];
end

assign PCSrc = Branch & (Zero ^ BNE);

endmodule

//MIPS_SCP.v
`timescale 1ns/1ns

module MIPS_SCP(
    input clk,
    input reset,
    output [31:0] PC,
    output [31:0] Instr,

    output [31:0] ALUResult,
    output [31:0] WriteData,
    output [31:0] ReadData,
    output RegWrite
);

    wire RegDst, ALUSrc, Jump, Jal, Jr, MemtoReg,
    PCSrc, Zero, MemWrite;
    wire [3:0] ALUControl;

    Datapath datapathcomp(
        .clk(clk),
        .reset(reset),
        .RegDst(RegDst),
        .RegWrite(RegWrite),
        .ALUSrc(ALUSrc),
        .Jump(Jump),
        .Jal(Jal),
        .Jr(Jr),
        .MemtoReg(MemtoReg),
        .PCSrc(PCSrc),
        .ALUControl(ALUControl),
        .ReadData(ReadData),
        .Instr(Instr),
        .PC(PC),
        .ZeroFlag(Zero),
        .datatwo(WriteData),
        .ALUResult(ALUResult)
    );

    ControlUnit controller(
        .Opcode(Instr[31:26]),
        .Func(Instr[5:0]),
        .Zero(Zero),
        .MemtoReg(MemtoReg),
        .MemWrite(MemWrite),
        .ALUSrc(ALUSrc),
        .RegDst(RegDst),
        .RegWrite(RegWrite),
        .Jump(Jump),
        .Jal(Jal),
        .Jr(Jr),

```

```

        .PCSrc(PCSrc),
        .ALUControl(ALUControl)
    );

    ram dmem(
        .clk(clk),
        .we(MemWrite),
        .adr(ALUResult),
        .din(WriteData),
        .dout(ReadData)
    );

    rom imem(
        .adr(PC),
        .dout(Instr)
    );

endmodule

//MIPS_SCP_tb.v for jaljrtest
`timescale 1ns/1ns

module MIPS_SCP_tb;

    // Inputs
    reg clk;
    reg reset;

    // Outputs from UUT
    wire [31:0] PC;
    wire [31:0] Instr;
    wire [31:0] ALUResult;
    wire [31:0] WriteData;
    wire [31:0] ReadData;
    wire RegWrite;

    // Instantiate Unit Under Test (UUT)
    MIPS_SCP uut (
        .clk(clk),
        .reset(reset),
        .PC(PC),
        .Instr(Instr),
        .ALUResult(ALUResult),
        .WriteData(WriteData),
        .ReadData(ReadData),
        .RegWrite(RegWrite)
    );

    // Clock generation
    initial clk = 0;
    always #50 clk = ~clk; // 100ns period

    // Monitor to display important signals
    initial begin
        $monitor("Time=%0t | PC=%h | Instr=%h | ALUResult=%h | WriteData=%h | ReadData=%h | RegWrite=%b",
            $time, PC, Instr, ALUResult, WriteData, ReadData, RegWrite);
    end

    // Test sequence
    initial begin
        // Initialize
        clk = 0;
        reset = 1;

        // Apply reset
        #100;
        reset = 0;

        // Run simulation long enough for JAL/JR
        execution
        #1000;

        // Check values in registers after function call
        $display("\n=== JAL/JR Test Results ===");
        $display("Register $a0 = %d (expected 5)",
            uut.datapathcomp.RF.register[4]);
        $display("Register $a1 = %d (expected 10)",
            uut.datapathcomp.RF.register[5]);
        $display("Register $v0 = %d (expected 15)",
            uut.datapathcomp.RF.register[2]);
    end
endmodule

```



```

    $display("Register $ra = %h (return
address)", uut.datapathcomp.RF.register[31]);

```

```

    $finish;
end

```

```

// VCD file for waveform viewing
initial begin
    $dumpfile("mips_scp_jal.vcd");
    $dumpvars(0, MIPS_SCP_tb);
end

```

```
endmodule
```

```
//MIPS_SCP_tb.v for min max mean
```

```
`timescale 1ns/1ns
```

```
module MIPS_SCP_tb;
```

```

// Inputs
reg clk;
reg reset;

```

```

// Outputs from uut
wire [31:0] PC;
wire [31:0] Instr;
wire [31:0] ALUResult;
wire [31:0] WriteData;
wire [31:0] ReadData;
wire RegWrite;

```

```

// Instantiation of Unit Under Test
MIPS_SCP uut (
    .clk(clk),
    .reset(reset),
    .PC(PC),
    .Instr(Instr),
    .ALUResult(ALUResult),
    .WriteData(WriteData),
    .ReadData(ReadData),
    .RegWrite(RegWrite)
);

```

```

// Clock generation
always #50 clk = ~clk;

```

```

// Monitor to display important signals
initial begin
    $monitor("Time=%0t  PC=%h  Instr=%h
ALUResult=%h  WriteData=%h  ReadData=%h
RegWrite=%b",
        $time, PC, Instr, ALUResult, WriteData,
        ReadData, RegWrite);
end

```

```
// Test sequence
```

```

initial begin
    // Initialize signals
    clk = 0;
    reset = 1;

```

```

// Apply reset
#100;
reset = 0;

```

```

// Run for enough cycles to execute the
program
#10000;

```

```

// Display final results
$display("\n===  Min/Max/Avg  Results
===");
$display("Expected:   Min=1,   Max=10,
Sum=55, Avg=5");
$display("Actual Results:");
$display("Register  $s0  (Min):  %d",
uut.datapathcomp.RF.register[16]); // $s0 =
reg16
$display("Register  $s1  (Max):  %d",
uut.datapathcomp.RF.register[17]); // $s1 =
reg17
$display("Register  $s2  (Sum):  %d",
uut.datapathcomp.RF.register[18]); // $s2 =
reg18

```

```

    $display("Register   $s3   (Avg):   %d",
uut.datapathcomp.RF.register[19]); // $s3 =
reg19

```

```

    $finish;
end
// VCD file generation for waveform viewing
initial begin
    $dumpfile("mips_scp.vcd");
    $dumpvars(0, MIPS_SCP_tb);
end

```

```
endmodule
```

```
//insttest2.s (assembly code for min max mean)
```

```
.data
```

```
newline: .ascii "\n"
```

```
.text
```

```
main:
```

```
    # Load numbers into $t0-$t9
```

```
    li $t0, 1
```

```
    li $t1, 2
```

```
    li $t2, 3
```

```
    li $t3, 4
```

```
    li $t4, 5
```

```
    li $t5, 6
```

```
    li $t6, 7
```

```
    li $t7, 8
```

```
    li $t8, 9
```

```
    li $t9, 10
```

```
# ----- Min -----
```

```
move $s0, $t0    # min = first value
```

```
move $s1, $t0    # max = first value
```

```
move $s2, $zero  # sum = 0
```

```
slt $a0, $t1, $s0
```

```
beq $a0, $zero, check2
```

```
move $s0, $t1
```

```
check2:
```

```
slt $a0, $t2, $s0
```

```
beq $a0, $zero, check3
```

```
move $s0, $t2
```

```
check3:
```

```
slt $a0, $t3, $s0
```

```
beq $a0, $zero, check4
```

```
move $s0, $t3
```

```
check4:
```

```
slt $a0, $t4, $s0
```

```
beq $a0, $zero, check5
```

```
move $s0, $t4
```

```
check5:
```

```
slt $a0, $t5, $s0
```

```
beq $a0, $zero, check6
```

```
move $s0, $t5
```

```
check6:
```

```
slt $a0, $t6, $s0
```

```
beq $a0, $zero, check7
```

```
move $s0, $t6
```

```
check7:
```

```
slt $a0, $t7, $s0
```

```
beq $a0, $zero, check8
```

```
move $s0, $t7
```

```
check8:
```

```
slt $a0, $t8, $s0
```

```
beq $a0, $zero, check9
```

```
move $s0, $t8
```

```
check9:
```

```
slt $a0, $t9, $s0
```

```
beq $a0, $zero, max_calc
```

```
move $s0, $t9
```

```
# ----- Max -----
```

```
max_calc:
```

```
move $s1, $t0    # max = first value
```

```
slt $s4, $s1, $t1
```

```
beq $s4, $zero, max2
```

```
move $s1, $t1
```

```
max2:
```

```
slt $s4, $s1, $t2
```

```
beq $s4, $zero, max3
```

```
move $s1, $t2
```

```
max3:
```

```
slt $s4, $s1, $t3
```

```

    beq $s4, $zero, max4
    move $s1, $t3
max4:
    slt $s4, $s1, $t4
    beq $s4, $zero, max5
    move $s1, $t4
max5:
    slt $s4, $s1, $t5
    beq $s4, $zero, max6
    move $s1, $t5
max6:
    slt $s4, $s1, $t6
    beq $s4, $zero, max7
    move $s1, $t6
max7:
    slt $s4, $s1, $t7
    beq $s4, $zero, max8
    move $s1, $t7
max8:
    slt $s4, $s1, $t8
    beq $s4, $zero, max9
    move $s1, $t8
max9:
    slt $s4, $s1, $t9
    beq $s4, $zero, sum_calc
    move $s1, $t9

# ----- Sum -----
sum_calc:
    add $s2, $t0, $t1
    add $s2, $s2, $t2
    add $s2, $s2, $t3
    add $s2, $s2, $t4
    add $s2, $s2, $t5
    add $s2, $s2, $t6
    add $s2, $s2, $t7
    add $s2, $s2, $t8
    add $s2, $s2, $t9

move $a0, $s2 # dividend = sum (55)
li $a1, 10    # divisor = 10
jal division_sub

```

```

nop
move $s3, $v0
li $v0, 10
nop

division_sub:
    move $v0, $zero # quotient = 0
    move $v1, $a0   # remainder = dividend
division_loop:
    slt $t1, $v1, $a1 # use $t1 instead of $t0
    bne $t1, $zero, division_done
    sub $v1, $v1, $a1
    addiu $v0, $v0, 1
    j division_loop
division_done:
    jr $ra
    nop

//insttest2.s (assembly code for Jal Jr test)
.text
main:
    li $a0, 5    # Load 5 into $a0
    li $a1, 10   # Load 10 into $a1
    jal add_numbers # Call add_numbers
    nop
    j end        # Infinite loop

# Function to add $a0 + $a1 and store in $v0
add_numbers:
    add $v0, $a0, $a1
    jr $ra      # Return to main

end:
    j end        # Infinite loop

```